


Week 8 Cribsheet

NOTES: 17, 17B

CHARGE SHARING

When useful: to analyze circuits with capacitors and switches

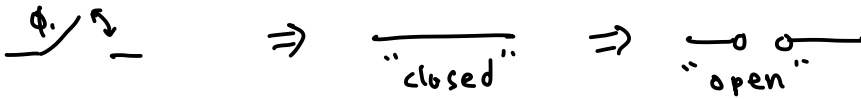switch: a circuit elt that "switches" between short/open



key principles of charge sharing: ★ important:

- charge cannot move through capacitor plates
- charge is conserved in floating nodes

floating node: a node that always ends in $\left\{ \begin{array}{l} \text{open circuit} \\ \text{capacitor} \end{array} \right.$

↳ aka. charge cannot enter or leave

set of phases ϕ_1, ϕ_2, \dots . Each one closes/opens some switches

STEPS


1. label capacitors with voltages and polarities (+/-)
2. draw the circuit versions in each phase ϕ_i
3. identify the floating nodes in these phases
4. amount of charge on floating nodes is invariant, write eqns
5. use eqn in step 4 to solve for desired quantity

CAPACITIVE TOUCHSCREEN

at each pixel:



without touch

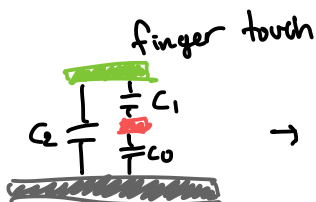


with touch

$$\rightarrow C_{eq} = C_0 + C_1 || C_2$$

each combination of red/gray bars represents a (x,y) pixel

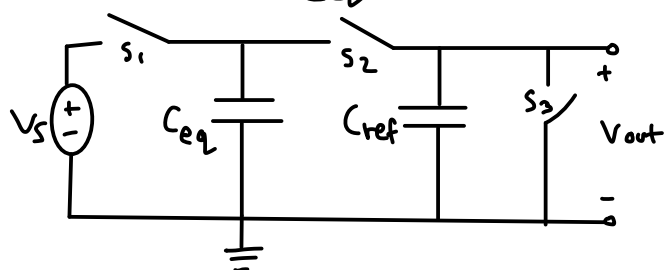circuit to measure C_{eq} : (can solve w charge sharing)




	ϕ_1	ϕ_2
S_1	closed	open
S_2	open	closed
S_3	closed	open

solving for C_{eq} , we get
$$V_{out} = \frac{C_{eq}}{C_{eq} + C_{ref}} V_s$$

(V_{out} is an observable property and C_{ref} , V_s constant)

want to know whether C_{eq} has changed (indicating touch)

connect V_{out} to a **comparator**:

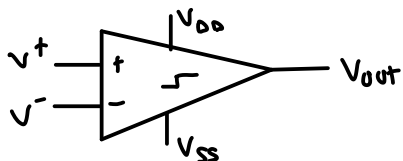

$$V_{out} = \begin{cases} V_{DD} & \text{if } v^+ > v^- \\ V_{SS} & \text{if } v^+ < v^- \end{cases}$$