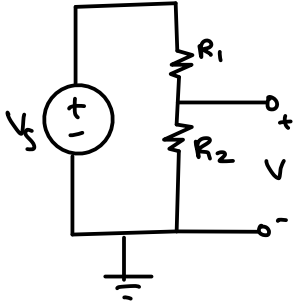


Week 6 Cribsheet

NOTES: 12, 13, 14

VOLTAGE DIVIDER

When useful: converting a larger voltage into a smaller one



$$V = \frac{R_2}{R_1 + R_2} V_S$$

$$\text{also, } V_{R_1} = \frac{R_1}{R_1 + R_2} V_S$$

voltage is "divided" into two weighted V 's.

★ same behavior w/ two inverting amps

1D RESISTIVE TOUCHSCREEN

Resistivity ρ (greek letter "rho") is a physical property of a resistor


$$R = \rho \frac{L}{A} = \rho \frac{\text{length}}{\text{sectional area}}$$



no touch



touch

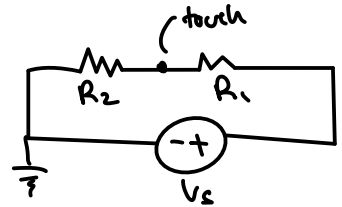


at touch point: $V_{\text{touch}} = \frac{R_2}{R_1 + R_2} V_S$ (voltage divider formula)

★ takeaway: knowing V
⇒ find location L_t !

$$\begin{aligned} &= \frac{\rho L_t / A}{\rho L_t / A + \rho L_r / A} V_S \\ &= \frac{L_t}{L_t + L_r} V_S \\ &= \frac{L_t}{L} V_S \end{aligned}$$

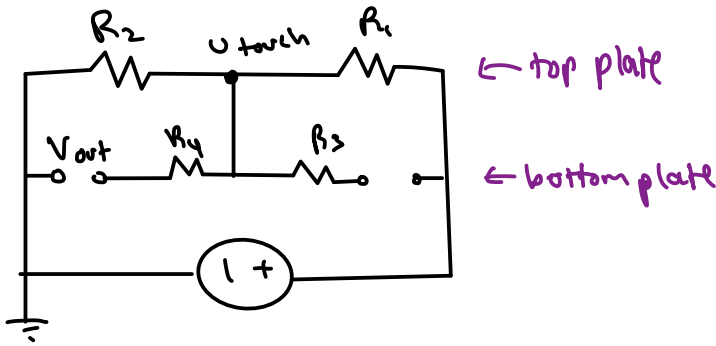
now, for bottom plate (to measure V_{touch} safely):



we can measure across V_{out} , because I thr R_4 is 0.

2D RESISTIVE TOUCHSCREEN

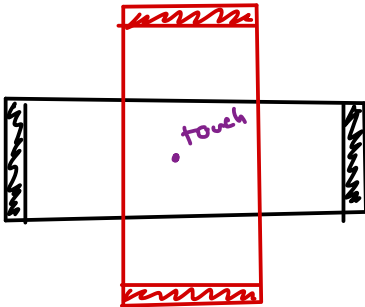an extension of the 1D touchscreen to measure (L_1, L_2) [pixel]



vertical

voltage source \Rightarrow red

voltmeter \Rightarrow black

horizontal

voltage source \Rightarrow black

voltmeter \Rightarrow red

Red plate:

Red :

$$V_3 = \frac{L_v}{L} V_S$$

Black :

$$V_3 = \frac{L_h}{L} V_S$$

Black plate:

